



COMSATS University of Islamabad

Vehari Campus

Name:

Fiaz Ahmad

Roll No:

FA24-BSE-127

Submitted by:

Syeda Zoupash Zahra


Subject:

Fundamentals of Digital Logic Design

Logic Equation.

$$Z = P \cdot Q + S \cdot S + P' + Q' \cdot S + S \cdot Q$$

7.5

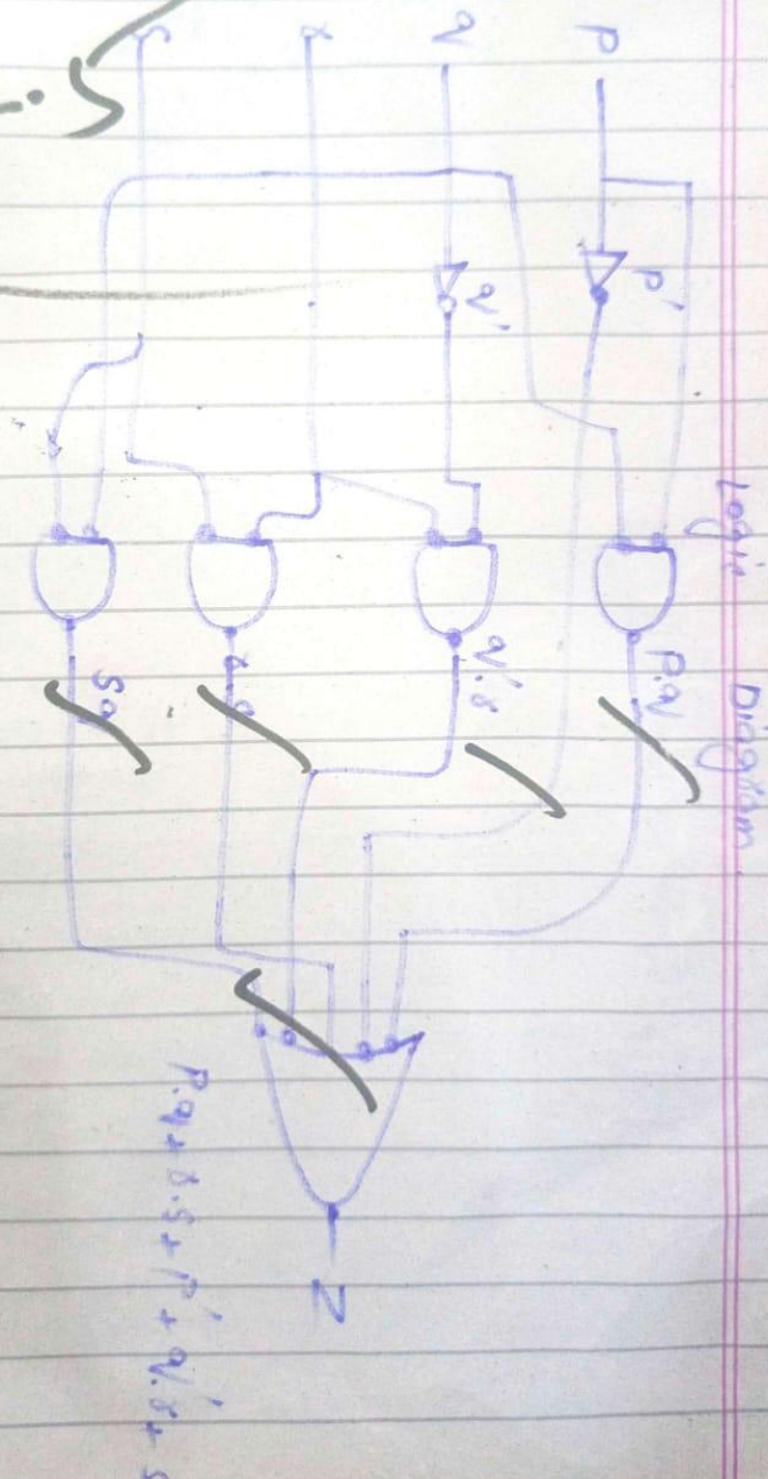

Fia3 Ahmad
FR24-BSE-127

